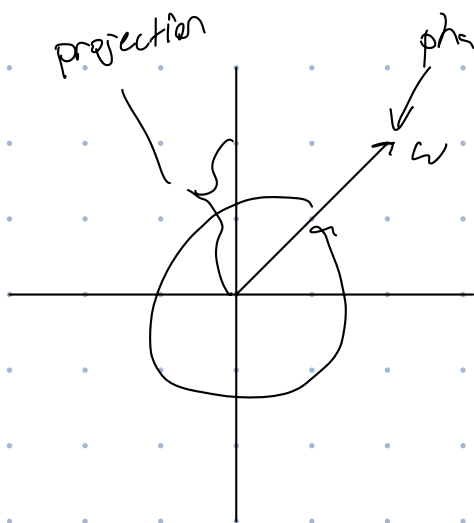



phasor




AC voltage is rotating arrow.

C/L act like a resistor in AC

Mutual inductance

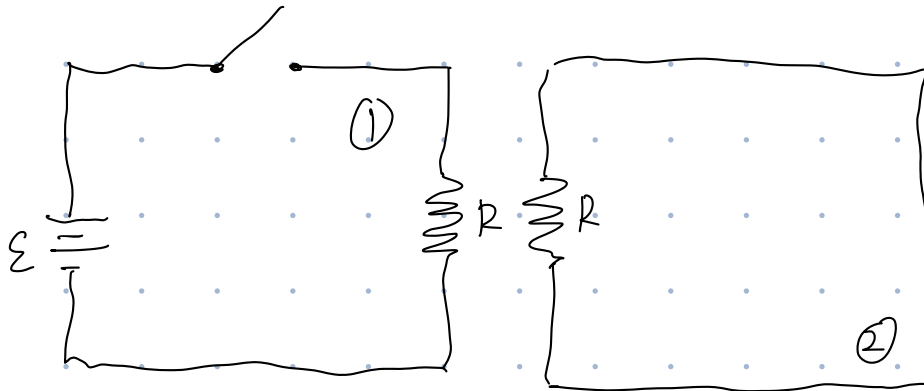

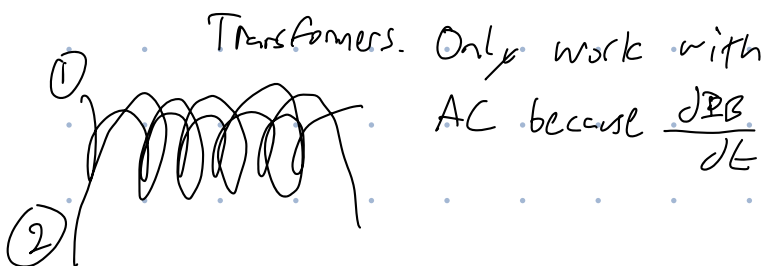• Close switch $\rightarrow I_1 \rightarrow \frac{d\Phi_B}{dt} \rightarrow I_2$ short term.



• Every circuit has an inductance & a capacitance.

The faster Φ_B changes the more back EMF.

$\uparrow \text{Hz} \rightarrow \uparrow \text{back EMF}$

Reactance - Resistance in AC

Impedance -

1) R: Joule resistance ($V=IR$)

• Doesn't change w/ frequency


2) X_C : Capacitive Reactance

• Changes w/ frequency

3) X_L : Inductive Reactance

• Changes w/ frequency

AC Circuits

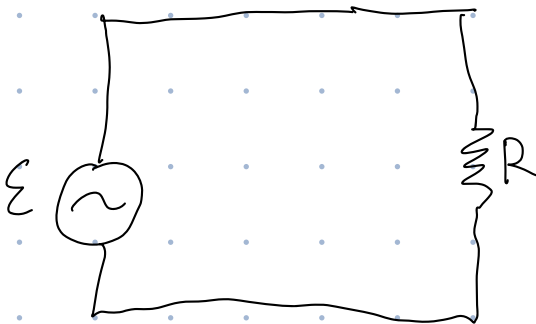

$$\epsilon = \epsilon_0 \sin \omega t$$

Find I & phase ϕ between I & ϵ ?

Loop:

$$\epsilon - V_R = 0$$

$$\epsilon_0 \sin \omega t - IR = 0$$

$$I = \frac{\epsilon_0}{R} \sin \omega t$$

Denominator is always your reactance terms.

I & ϵ are in phase.


$$\phi = 0^\circ$$

• Reach their max @ the same time = in phase

Ex 2: Capacitive Reactance

FT then $\uparrow I$

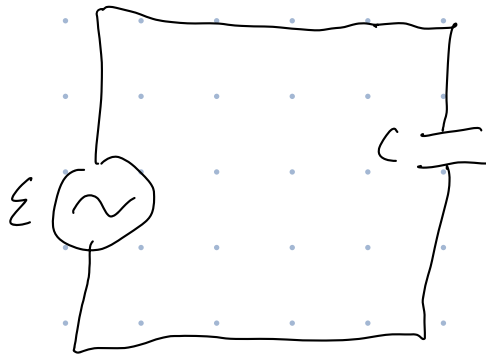because I is large when you first start charging capacitor



Loop:

$$\Sigma - V_C = 0$$

$$I = \frac{dQ}{dt}$$

$$\Sigma_0 \sin \omega t - \frac{Q}{C} = 0$$

$$C \Sigma_0 \sin \omega t = Q$$

I & Σ are $\phi = 90^\circ$ out of phase.


$$\omega C \Sigma_0 \cos \omega t = \frac{dQ}{dt}$$

$$i = \frac{dQ}{dt} = \frac{2\pi}{T} = 2\pi f = \frac{\Sigma_0}{\frac{1}{\omega C}} \cos \omega t = I$$

x_C

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

Ex 3:

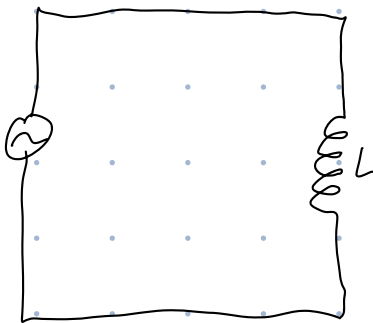

loop:

$$\Sigma - V_L = 0$$

$$\Sigma_0 \sin \omega t - L \frac{dI}{dt} = 0$$

$$\frac{\Sigma_0}{L} \sin \omega t = \frac{dI}{dt}$$

I is -90° out of phase with Σ

$$\int \frac{\Sigma_0}{L} \sin \omega t dt = \int dI$$

$$-\frac{\Sigma_0}{L\omega} \cos \omega t = I$$

x_L in Ω

$$X_L = \omega L = 2\pi f L$$



$$\uparrow H_z \rightarrow \uparrow \frac{d\Phi_B}{dt} \rightarrow \uparrow X_L$$

L - Opposes any change in I

C - Opposes any change in V

derive inductive reactance.
or capacitive reactance,

LCR series circuit

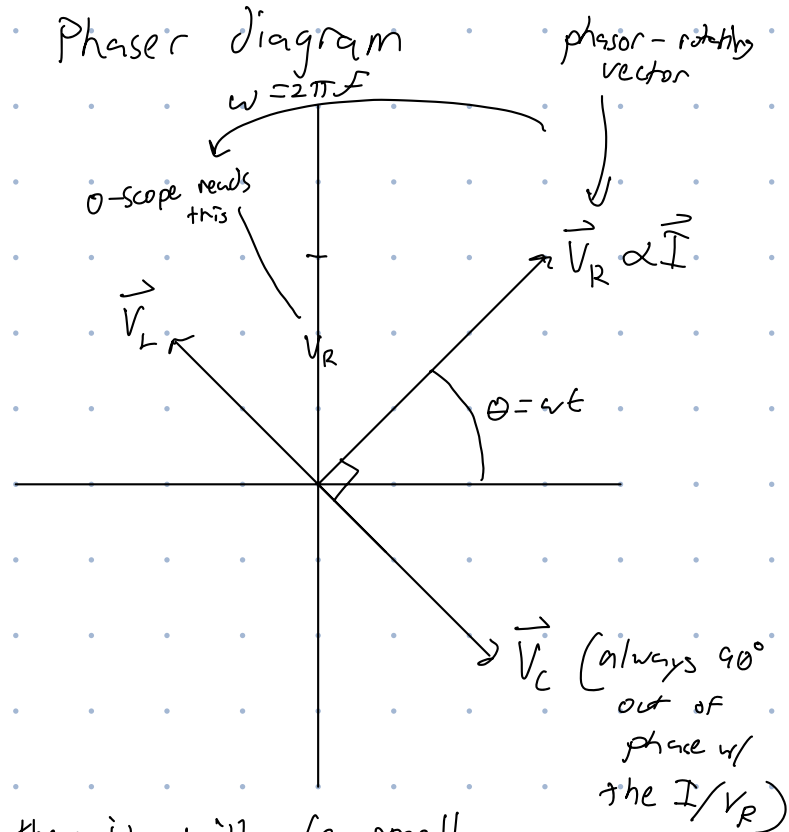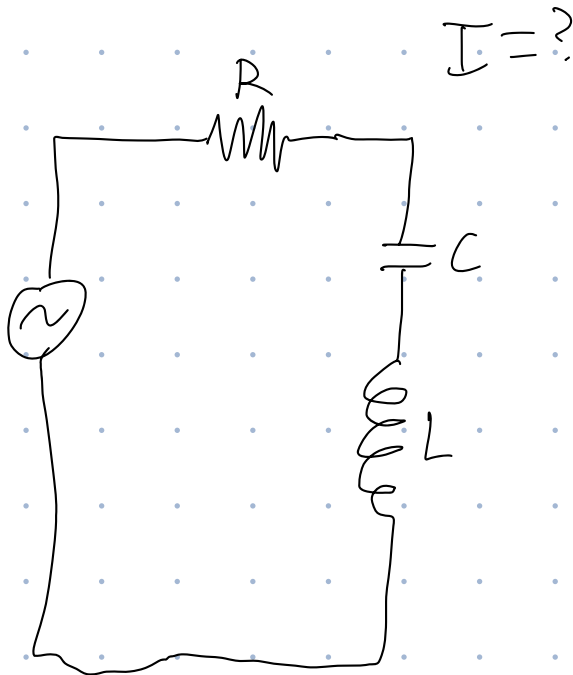

at f where the I will be big, but others it will be small.

Z - impedance - Joule resistance + Reactances.

ELI the ICEman


L - Inductor

C - Capacitor

Voltage (\mathcal{E}) leads
the current

Current leads
the voltage (\mathcal{E})

say $\vec{V}_L > \vec{V}_C$


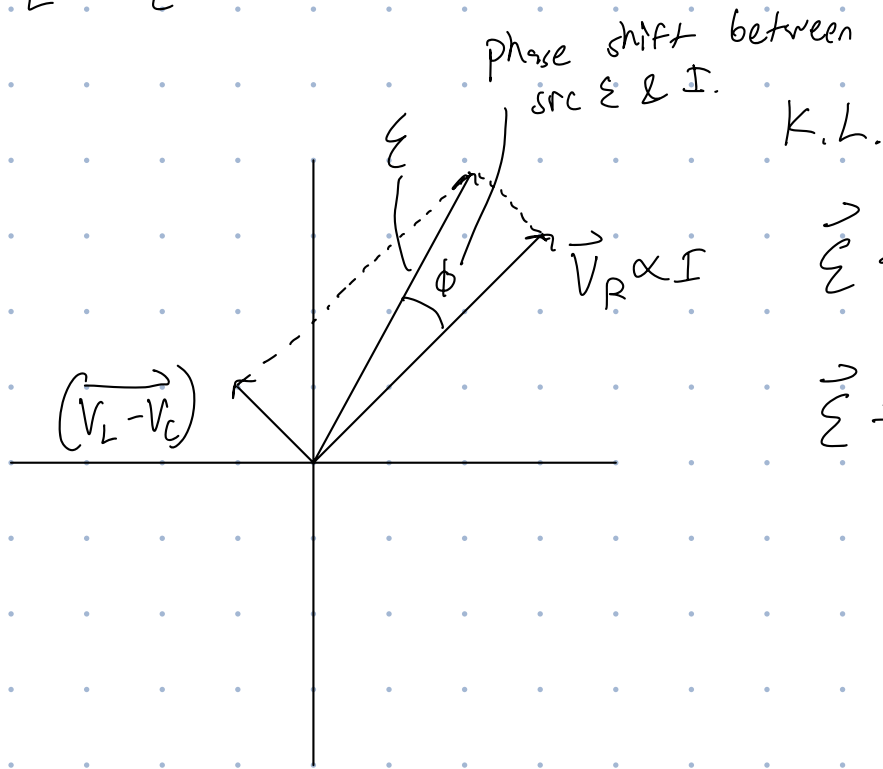


$$\vec{\Sigma} - \vec{V}_L - \vec{V}_R - \vec{V}_C = 0$$

$$\vec{\Sigma} = \vec{V}_L + \vec{V}_R + \vec{V}_C = 0$$

Find ϕ

L-R circuit series

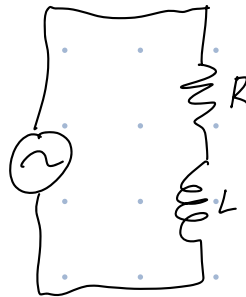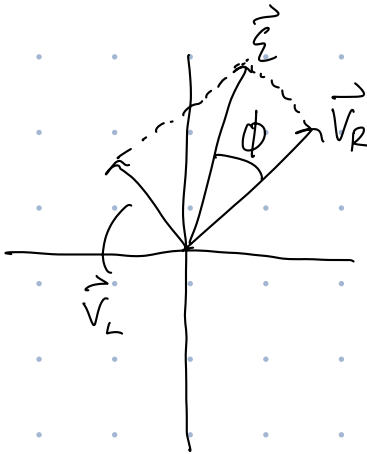

$$\Sigma - V_R - V_L = 0$$



$$V_L = I X_L$$


$$V_R = I R$$

$$\tan \phi = \frac{\text{OPP}}{\text{adj}} = \frac{V_L}{V_R} = \frac{I X_L}{I R}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$= \tan^{-1} \left(\frac{2\pi f L}{R} \right)$$

L-C-R circuit

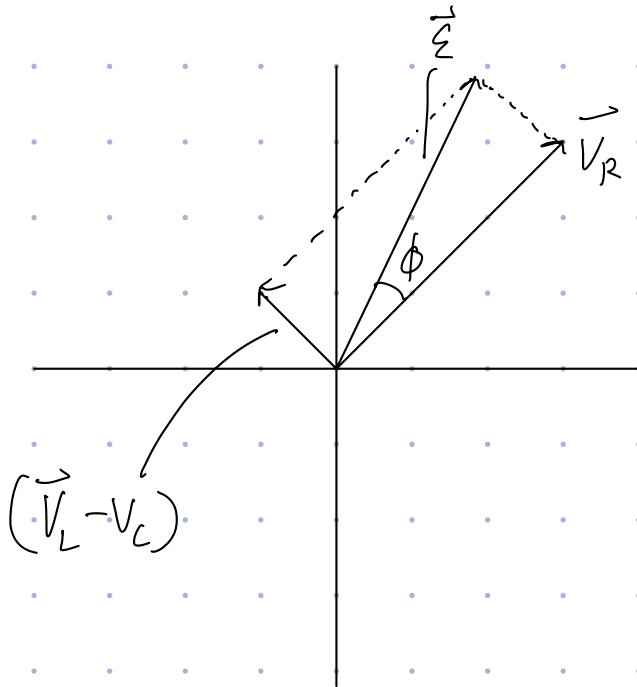

Pythagorean.

Ohm's Law whole circuit

$$E = \sqrt{(V_L - V_C)^2 + V_R^2}$$

$$IZ = \sqrt{(IX_L - IX_C)^2 + (IR)^2}$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

$$Z = \sqrt{\left(\omega L - \frac{1}{\omega C}\right)^2 + R^2}$$

Z is a min when $\omega L - \frac{1}{\omega C} = 0$

So current is a max

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 LC = 1$$

$$\omega^2 = \frac{1}{LC}$$

$$f = \frac{1}{2\pi\sqrt{LC}} \quad \text{Resonance frequency}$$